

Learning Electricity and Circuits Worksheet


Name:

Date:


Class:



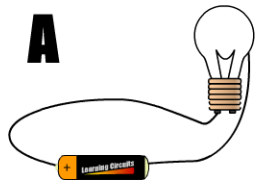
For each of the circuits below tick if you think it will work or not




Work Not Work

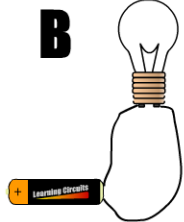

Work Not Work

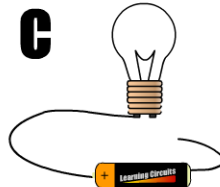


Work Not Work

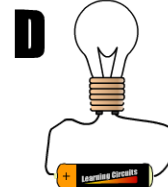


Work Not Work

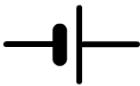Label the symbols with the correct component



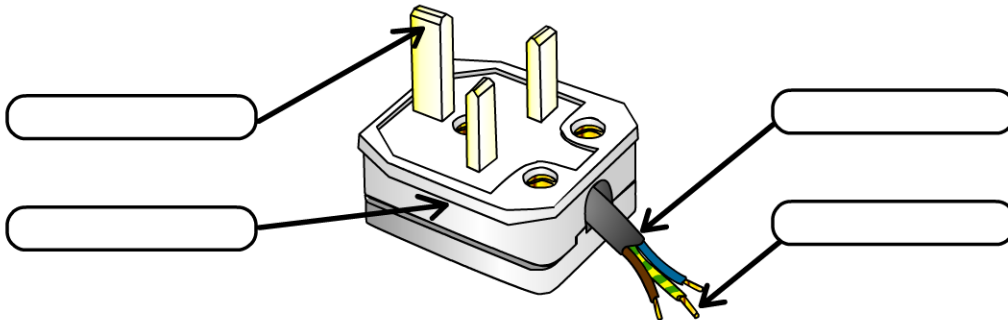Look at the diagram of a plug, can you label the conductors and insulators?



Once you have completed this worksheet hand it in to your teacher or parent. You can also keep it for revision